

Registers and Counter


- The flip-flops are essential component in clocked sequential circuits.
- Circuits that include flip-flops are usually classified by the function they perform. Two such circuits are registers and counters.
- An n -bit register consists of a group of n flip-flops capable of storing n bits of binary information.

Registers

- In its broadest definition, a register consists a group of flip-flops and gates that effect their transition.
 - The flip-flops hold the binary information.
 - The gates determine how the information is transferred into the register.
- Counters are a special type of register.
- A counter goes through a predetermined sequence of states.

Registers

 
- Fig shows a register constructed with four D-type flipflops.
- “Clock” triggers all flipflops on the positive edge of each pulse.
- “Clear” is useful for clearing the register to all 0’s prior to its clocked operation.



Register with Parallel Load

- A clock edge applied to the C inputs of the register of Fig. will load all four inputs in parallel.
- For synchronism, it is advisable to control the operation of the register with the D inputs rather than controlling the clock in the C inputs of the flip-flops.
- A 4-bit register with a load control input that is directed through gates and into the D inputs of the flip-flops is shown in Fig.

Register with Parallel Load

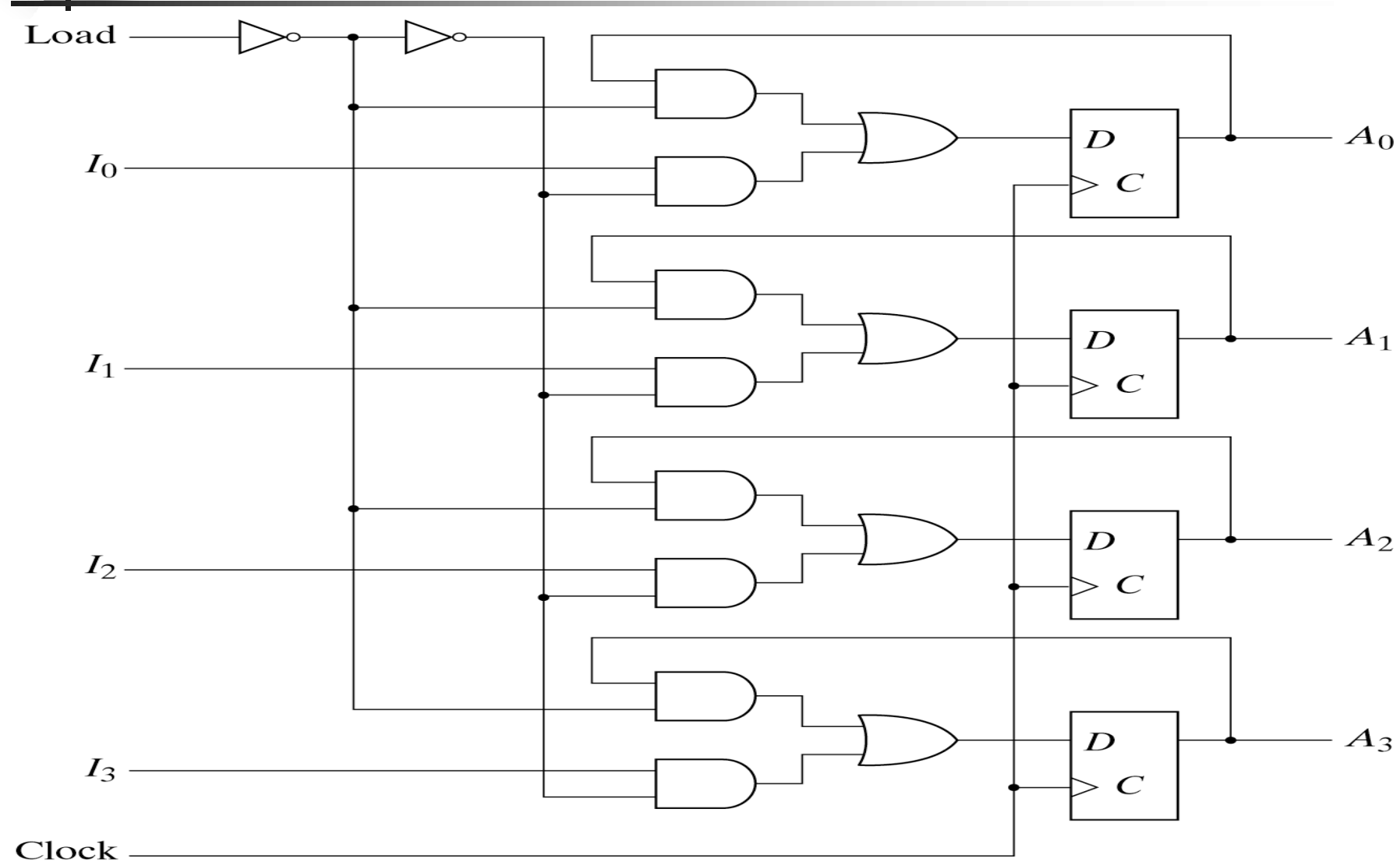

Register with Parallel Load

- When the load input is 1 , the data in the four inputs are transferred into the register with next positive edge of the clock.
- When the load input is 0 ,the outputs of the flip-flops are connected to their respective inputs.
- The feedback connection from output to input is necessary because the D flip-flops does not have a “no change” condition.

Shift Registers

- A register capable of shifting its binary information in one or both direction is called a *shift register*.
- All flip-flops receive common clock pulses, which activate the shift from one stage to the next.
- The simplest possible shift register is one that uses only flip-flops, as shown in Fig.

Shift Registers

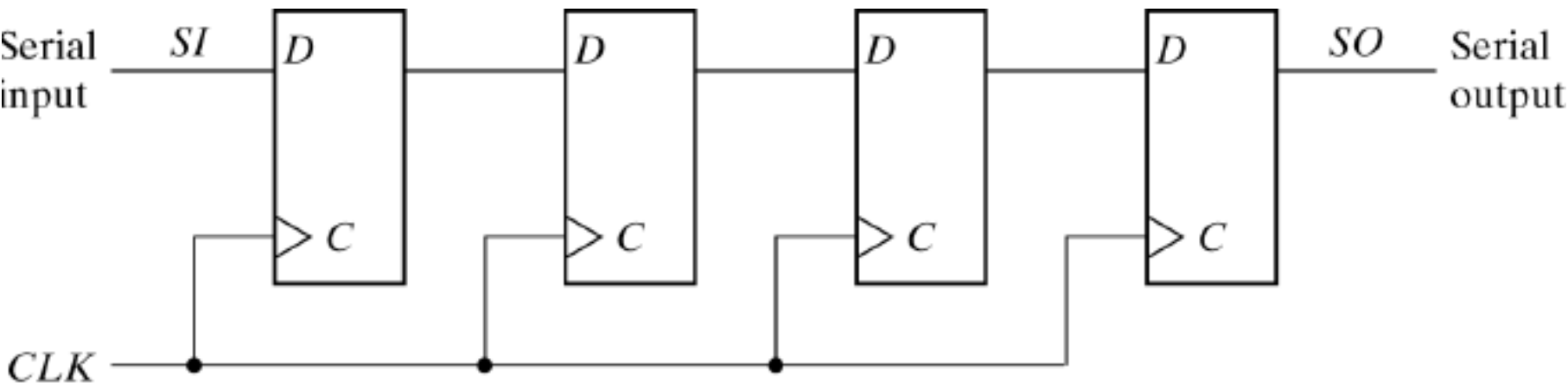


Fig. 4-Bit Shift Register

Shift Registers


- Each clock pulse shifts the contents of the register one bit position to the right.
- The *serial input* determines what goes into the leftmost flip-flop during the shift.
- The *serial output* is taken from the output of the rightmost flip-flop.

Counters


- A register that goes through a prescribed sequence of states upon the application of input pulse is called a counter.
- A counter that follows the binary number sequence is called a binary counter.
- Counters are available in two categories
 - Ripple (Asynchronous) counters
 - Parallel (Synchronous) counters

Binary Ripple Counter

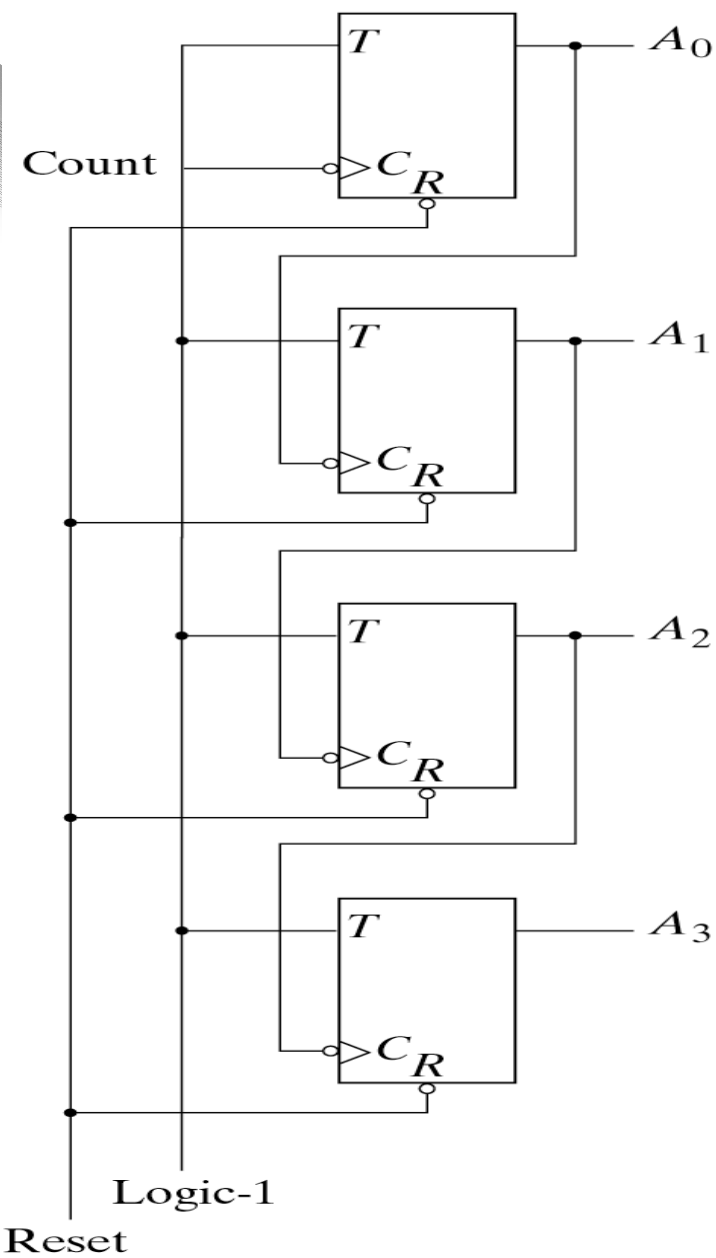- The output of each flip-flop is connected to the C input of the next flip-flop in sequence.
- The flip-flop holding the last significant bit receives the incoming count pulse.
- A complementing flip-flop can be obtained from:
 - JK flip-flop with the J and K inputs tied together.
 - T flip-flop
 - D flip-flop with the complement output connected to the D input. [Fig.]



(a) With T flip-flops

 


(b) With D flip-flops

Synchronous Counters

- Synchronous counters are different from ripple counters in that clock pulses are applied to the inputs of all flip-flops.
- A common clock triggers all flip-flops simultaneously rather than one at a time in succession as in a ripple counter.


Binary Counter

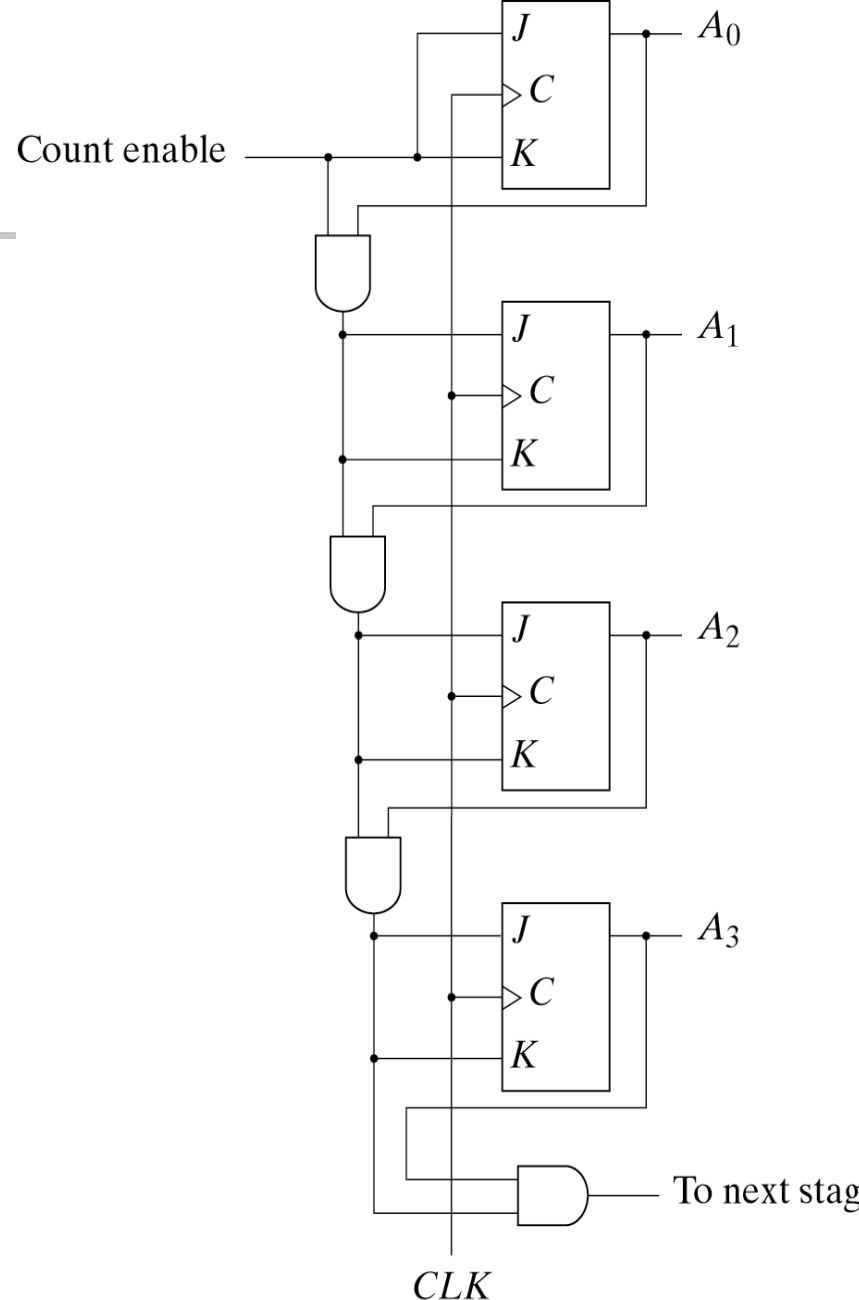- The design of a synchronous binary counter is so simple that is no need to go through a sequential logic design process.
- Synchronous binary counters have a regular pattern and can be constructed with complementing flip-flop and gates



Binary Counter with Parallel Load

 - Counters employed in digital systems quite often require a parallel load capability for transferring an initial binary number into the counter prior to count operation.
- The input load control when equal to 1 disables the count operation and causes a transfer of data from the four data inputs into the four flip-flops [Fig.]



Binary Counter with Parallel Load

Table
Function Table for the Counter of Fig.

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1		1	X	Load inputs
1		0	1	Count next binary state
1		0	0	No change