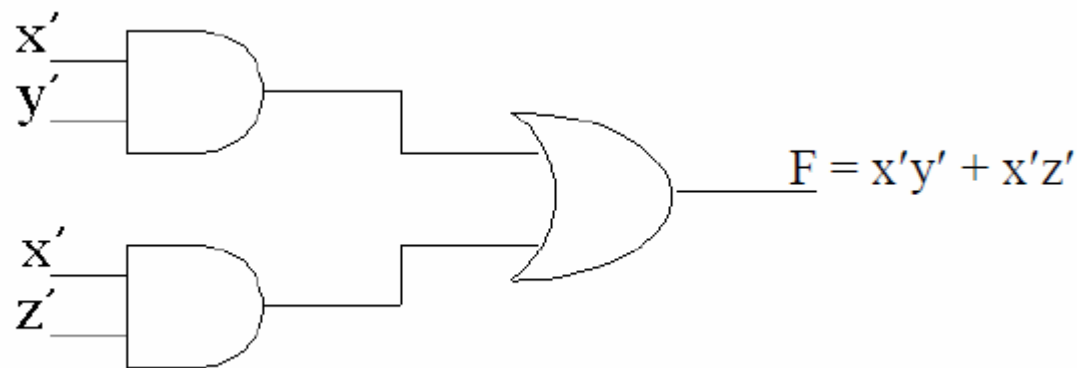


Numerical on K-maps Half and Full Adder

Q1: Design a combinational circuit with three inputs and one output. The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise.


x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		$\longleftrightarrow y$			
	x\yz	00	01	11	10
	0	1	1		1
$\updownarrow x$	1				



Q2: A majority function is generated in a combinational circuit when the output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise. Design a three-input majority function.

x y z	F
0 0 0	0
0 0 1	0
0 1 0	0
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	1
1 1 1	1

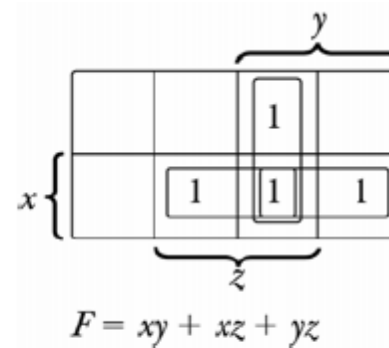

Q3: Design a combinational circuit with three inputs x, y, z and three outputs A, B, C.
When the binary input is 0, 1, 2, or 3, the binary output is one greater than the input.
When the binary input is 4, 5, 6, or 7, the binary output is one less than the input.

x	y	z	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

		$\longleftrightarrow y$			
$x \backslash yz$	00	01	11	10	
0			1		
1		1	1	1	

$$A = xy + xz + yz$$

		$\longleftrightarrow y$			
	x\yz	00	01	11	10
	0		1		1
$\updownarrow x$	1	1		1	

$$B = x \oplus y \oplus z \quad C = z'$$

